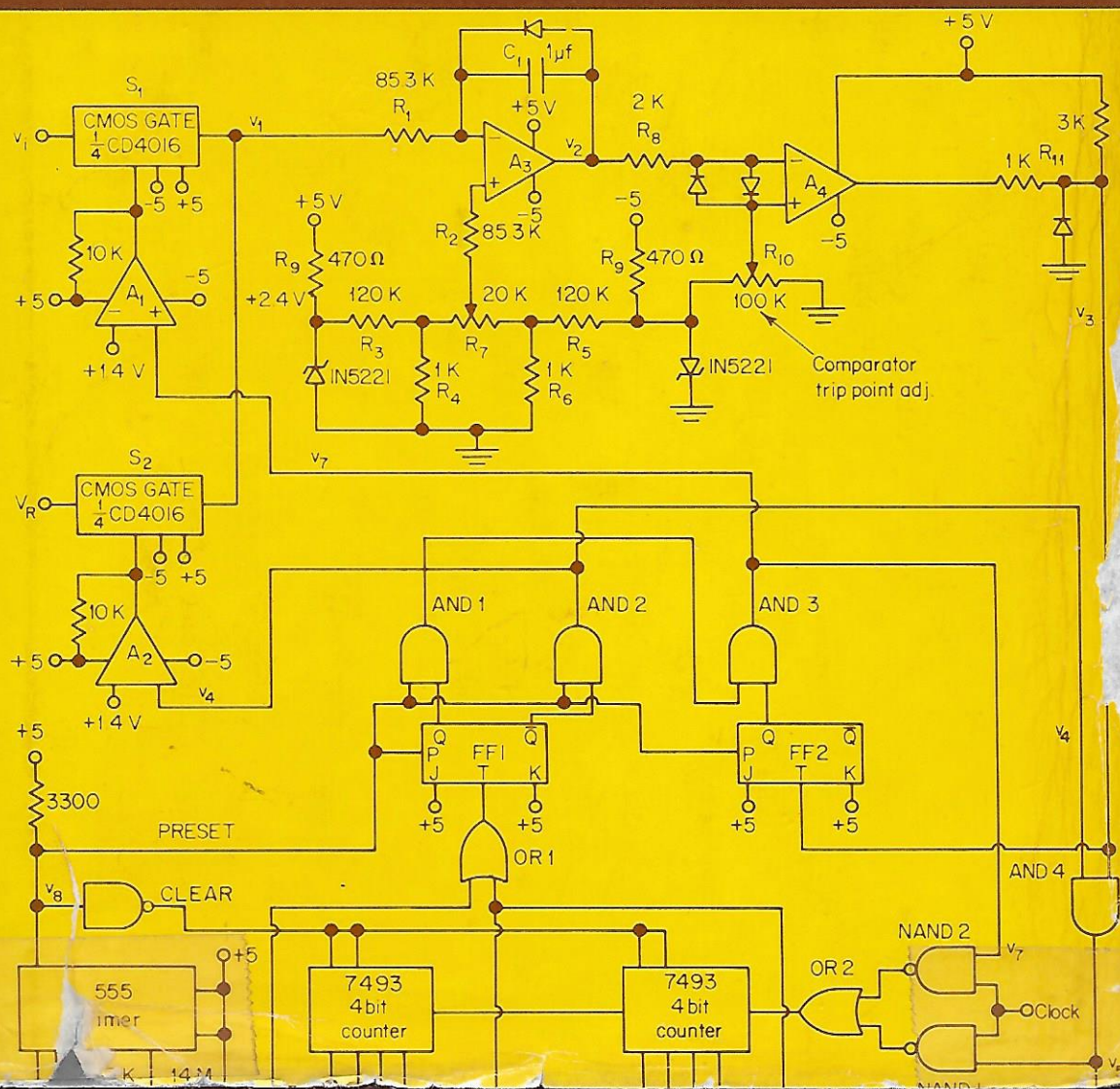


OPERATIONAL AMPLIFIER CIRCUIT DESIGN



Chapter 21

Oscillators

INTRODUCTION

In this chapter we will provide detailed design information on two popular oscillator circuits. First to be described is the popular Wien-bridge sine-wave oscillator. The circuit presented will be a superior design which has controlled amplitude and frequency stability. The second circuit presented is a voltage-controlled square-wave generator.

Other types of oscillators are presented elsewhere in this handbook. Chapter 20 contains detailed design information on the basic square-wave generator. Several types of waveform generators are presented in Chap. 27.

21.1 WIEN-BRIDGE SINE-WAVE OSCILLATOR

ALTERNATE NAMES Phase-shift oscillator, AGC oscillator, sine-wave generator.

EXPLANATION OF OPERATION A Wien bridge is made up of a series RC circuit in one branch of a bridge and a parallel RC circuit in another branch. In the Wien-bridge oscillator shown in Fig. 21.1 these components are R_1 , R_2 , C_1 , and C_2 . The circuit will oscillate at that frequency where the phase of V_1 is identical to the phase of V_o . This frequency, in terms of circuit components, is

$$f_o = \frac{1}{2\pi(R_1 R_2 C_1 C_2)^{1/2}}$$

Oscillation cannot be sustained unless the positive feedback through R_1 , R_2 , C_1 , and C_2 is exactly equal to the forward gain controlled by R_3 , R_5 , and R_6 . The feedback factor (gain from V_o to V_1) through the Wien bridge is (at f_o)

$$A_f = 1 + \frac{R_2}{R_1} + \frac{C_1}{C_2}$$

The forward gain of the amplifier is (at dc)

$$A_{vc} = 1 + \frac{R_3}{R_5} + \frac{R_3 R_4}{R_5 R_1}$$

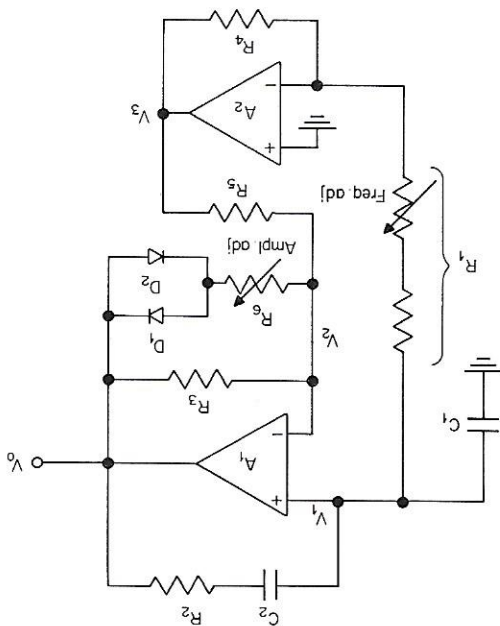


Fig. 21.1 A Wien-bridge oscillator which requires only one component for tuning.

These gains will be equal if we satisfy the following equalities:

$$R_2 = R_3 = R_4 = R_5 \quad (C_1 = C_2) \quad (\text{in practice } R_3 \text{ is made 5 to 10 percent higher})$$

In basic Wien-bridge oscillators R_1 is returned to ground. In the present circuit, however, it is returned to a virtual ground at the inverting input of A_2 . This additional circuit, composed of A_2 , R_1 , and R_5 , is added so that a single part R_1 can be used for tuning. The A_2 circuit forces the positive feedback to equal the negative feedback for all values of R_1 . The circuit composed of D_1 , D_2 , and R_6 is used to maintain V_0 amplitude stability. If V_0 tries to increase owing to load changes, diodes D_1 and D_2 conduct harder. This makes R_5 appear to be smaller, which lowers the gain of A_1 and restores V_0 to its correct value. The diodes keep R_6 out of the circuit until a firm oscillation is present. Otherwise the circuit would have too much negative feedback and would not start.

If R_1 is to be variable, its limits should be controlled. The minimum R_1 is constrained by the maximum available gain of A_2 at f_0 . Equation 5 must be satisfied, so that the gain of the A_2 circuit ($-R_5/R_1$) will never attempt to exceed the open-loop gain of A_2 at f_0 . Conversely, very large values of R_1 will cause A_1 to have a dc output offset of $I_{B1}R_1$. The maximum R_1 is therefore constrained by the maximum allowable output offset.

DESIGN PARAMETERS

Parameter	Description
A_1	Op amp which oscillates
A_2	Op amp used to keep gain of A_1 constant as R_1 is adjusted
A_f	Feedback factor V_1/V_0 of Wien bridge

Parameter	Description
A_{ve}	Gain of A_1 circuit from V_1 to V_o assuming Wien bridge is not present
C_1 to C_2	Determines frequency of oscillation along with R_1 and R_2
D_1 to D_2	Used to control gain (and output amplitude) of A_1 circuit
f_o	Frequency of oscillation
f_{u2}	Unity-gain crossover frequency of A_2
I_{b1}	Input bias current of A_1
$R_1(\text{min})$	Fixed portion of R_1
$R_1(\text{max})$	Variable portion of R_1
R_2	Controls frequency of oscillation along with R_1 , C_1 , and C_2
R_3	Sets basic gain of A_1 circuit
R_4 to R_5	Controls effect of A_2 circuit on the gain of A_1 circuit
R_6	Used to adjust stability and also output amplitude (to a lesser extent)
V_1 to V_3	Voltages at various nodes in Fig. 21.1
V_o	Output voltage
ΔV_o	Output offset due to input bias current of A_1
$V^{(\pm)}$	Power-supply voltages

DESIGN EQUATIONS

Eq. No.	Description	Equation
1	Frequency of oscillation	$f_o = \frac{1}{2\pi(R_1 R_2 C_1 C_2)^{1/2}}$
2	Feedback factor of Wien bridge at f_o	$A_f(f_o) = \frac{V_1}{V_o} = 1 + \frac{R_2}{R_1} + \frac{C_1}{C_2}$
3	Gain of A_1 circuit from V_1 to V_o (assuming Wien bridge is disconnected) Recommended resistor values:	$A_{ve} = 1 + \frac{R_3}{R_5} + \frac{R_3 R_4}{R_5 R_1}$
4	R_1 (variable portion)	$R_1(\text{max}) \cong \frac{\Delta V_o(\text{max})}{I_{b1}}$
5	R_1 (fixed portion)	$R_1(\text{min}) \cong \left(\frac{R_4^2}{4\pi^2 R_2 C_1 C_2 f_{u2}^2} \right)^{1/3}$
6	R_2, R_4, R_5	$R_2 = R_4 = R_5 = [R_1(\text{max})]^{1/2}$
7	R_3	$R_3 \approx 1.1 R_2$
8	R_6	$R_6 \approx 100 R_3$
9	Recommended capacitor values C_1, C_2	$C_1 = C_2 = \frac{1}{2\pi f_o R_2}$
10	Maximum f_o	$f_o(\text{max}) \approx \left(\frac{f_{u2}}{4\pi^2 R_2 R_4 C_1 C_2} \right)^{1/3}$
11	Minimum f_o	$f_o(\text{min}) \approx \frac{1}{2\pi} \left[\frac{I_{b1}}{R_2 C_1 C_2 \Delta V_o(\text{max})} \right]^{1/2}$

DESIGN PROCEDURE

We begin by assuming the midband frequencies are most important. We then perform calculations to determine the maximum and minimum frequency limits of the oscillator.

DESIGN STEPS

- Step 1.** Compute a value for $R_1(\text{max})$ using Eq. 4.
- Step 2.** Sequentially apply Eqs. 6, 7, and 8 to determine the other resistor values.
- Step 3.** Determine nominal values for C_1 and C_2 using Eq. 9.
- Step 4.** Compute the fixed portion of R_1 using Eq. 5. The variable portion of R_1 should be a log-taper potentiometer if one wants a constant octave/degree control of frequency.
- Step 5.** Compute the approximate frequency limits expected from the oscillator using Eqs. 10 and 11.
- Step 6.** Double-check all previous calculations by computing f_o with Eq. 1 at $R_1(\text{min})$, $R_1(\text{max})$, and the square root of $R_1(\text{max})$.
- WIEN-BRIDGE-OSCILLATOR DESIGN EXAMPLE** An oscillator with a mid-range frequency of 1,000 Hz will be designed. The maximum output voltage (peak-to-peak) and output offset are specified. The op amps are also predetermined. We are asked to determine the upper- and lower-frequency limits of the oscillator.

Design Requirements

$$\begin{aligned} V_o &= \pm 10 \text{ V} \\ \Delta V_o(\text{max}) &= 0.1 \text{ V} \\ f_o(\text{midband}) &= 1,000 \text{ Hz} \\ A_1 \text{ and } A_2 &= \text{LM } 324 \\ V^{(\pm)} &= \pm 15 \text{ V} \end{aligned}$$

Device Data

$$\begin{aligned} f_{uz} &= 5 \times 10^5 \text{ Hz} \\ I_{b1} &= 3 \times 10^{-8} \text{ A} \end{aligned}$$

Step 1. The adjustable portion of R_1 is

$$R_1(\text{max}) = \frac{\Delta V_o(\text{max})}{0.1} = \frac{I_{b1}}{3 \times 10^{-8}} = 3.3 \text{ M}\Omega$$

Step 2. Equation 6 provides us with

$$R_2 = R_4 = R_5 = [R_1(\text{max})]^{1/2} = (3.3 \times 10^6)^{1/2} = 1,830 \Omega$$

Equation 7 is approximately

$$R_3 \approx 1.1 R_2 = 1.1(1,830) = 2,000 \Omega$$

R_6 is found from Eq. 8:

$$R_6 \approx 100 R_3 = 100(2,000) = 200 \text{ k}\Omega$$

Step 3. Equation 9 gives us nominal values for C_1 and C_2 :

$$C_1 = C_2 = \frac{1}{2\pi f_o R_2} = \frac{1}{2\pi(1,000)(1,830)} = 0.087 \mu\text{F}$$

The output will not be a pure sine wave unless these capacitors are closely matched.

Step 4. The fixed portion of R_1 is

$$\begin{aligned} R_1(\text{min}) &= \left(\frac{R_2^2}{4\pi^2 R_2 C_1 C_2 f_z^2} \right)^{1/3} \\ &= \left[\frac{1,830^2}{4\pi^2(1,830)(0.087 \times 10^{-6})(5 \times 10^5)^2} \right]^{1/3} = 29 \Omega \end{aligned}$$

Step 5. We now substitute data into Eqs. 10 and 11 to find the oscillator range:

$$f_o(\text{max}) = \left(\frac{f_{n2}}{4\pi^2 R_2 R_4 C_1 C_2} \right)^{1/3} \\ = \left[\frac{5 \times 10^5}{4\pi^2 (1,830)^2 (0.087 \times 10^{-6})^2} \right]^{1/3} = 7,900 \text{ Hz}$$

$$f_o(\text{min}) = \frac{1}{2\pi} \left[\frac{I_{b1}}{R_2 C_1 C_2 \Delta V_o(\text{max})} \right]^{1/2} \\ = \frac{1}{2\pi} \left[\frac{3 \times 10^{-8}}{(1,830)(0.087 \times 10^{-6})^2 0.1} \right]^{1/2} = 23.4 \text{ Hz}$$

Step 6. The oscillator frequency is computed using Eq. 1 along with the results of steps 1, 2, 3, and 4.

$$f_o(\text{min}) = \frac{1}{2\pi [R_1(\text{max}) R_2 C_1 C_2]^{1/2}} \\ = \frac{1}{2\pi [(3.3 \times 10^6) 1,830 (0.087 \times 10^{-6})^2]^{1/2}} = 23.4$$

$$f_o(\text{nom}) = \frac{1}{2\pi [R_1(\text{nom}) R_2 C_1 C_2]^{1/2}} \\ = \frac{1}{2\pi [1,830 (1,830) (0.087 \times 10^{-6})^2]^{1/2}} = 1,000 \text{ Hz}$$

$$f_o(\text{max}) = \frac{1}{2\pi [R_1(\text{min}) R_2 C_1 C_2]^{1/2}} \\ = \frac{1}{2\pi [29 (1,830) (0.087 \times 10^{-6})^2]^{1/2}} = 7,958 \text{ Hz}$$

REFERENCES

1. Brokaw, P.: FET Op Amp Adds New Twist to an Old Circuit, *EDN*, June 5, 1974, p. 75.
2. Coers, G.: MOSFET Network Minimizes Audio Oscillator Distortion, *Electronics*, Jan. 3, 1972, p. 85.
3. Widlar, R. J., and J. N. Giles: Avoid Over Integration, *Electron. Des.*, Feb. 1, 1966, p. 56.

21.2 VOLTAGE-CONTROLLED OSCILLATOR

ALTERNATE NAMES VCO, voltage-controlled pulse generator, voltage-to-frequency converter, V/F converter, VFC.

EXPLANATION OF OPERATION The op amp circuit is an integrator which is constantly attempting to drive its output terminal high. The rate at which the output slews high is

$$\frac{\Delta v_1}{\Delta t} = \frac{v_m}{R_1 C_1}$$